

Διάχυτα και ενσωματωμένα συστήματα

Τμήμα Μηχανικών Πληροφορικής και Υπολογιστών

Γιάννης Βογιατζής

Εισαγωγή στη VHDL

Genesis of VHDL

Κατάσταση στη δεκαετία του '80

- Πολλαπλές μέθοδοι design entry methods και γλώσσες περιγραφής υλικού
- Περιορισμένη ή μηδενική φορητότητα στα σχέδια μεταξύ CAD tools από διαφορετικούς vendors
- Στόχος: μείωση του χρόνου από design concept μέχρι το implementation από τους 18 μήνες στους 6 μήνες

VHDL

VHDL: γλώσσα περιγραφής υλικού

VHDL : **V**HSIC (**V**ery **H**igh **S**peed **I**ntegrated **C**ircuit) **H**ardware **D**escription **L**anguage

Naming and Labeling (1)

- VHDL is case insensitive

Example:

Names or labels

databus

Databus

DataBus

DATABUS

are all equivalent

Naming and Labeling (2)

1. Τα ονόματα αρχίζουν από (a-z or A-Z)
2. Χρησιμοποιούνται χαρακτήρες (a-z or A-Z) ψηφία (0-9) και underscore (`_`)
3. Δε χρησιμοποιούνται punctuation ή reserved characters (!, ?, ., &, +, -, etc.)
4. Δε χρησιμοποιούνται δύο ή περισσότερα underscore characters (`__`)
5. Όλα τα ονόματα σε ένα entity πρέπει να είναι μοναδικά

Valid or invalid?

7segment_display

A87372477424

Adder/Subtractor

/reset

And_or_gate

AND__OR__NOT

Kogge-Stone-Adder

Ripple&Carry_Adder

My adder

Free Format

- Η Vhdl είναι μια “free format” γλώσσα

Example:

```
if (a=b) then
```

or

```
if (a=b)           then
```

or

```
if (a =  
b) then
```

are all equivalent

Σχόλια

- Με “double dash”, i.e., “--”
 - Μπορούν να μπουν οπουδήποτε στη γραμμή
 - Ότι είναι στην ίδια γραμμή είναι σχόλιο


Examples:

-- main subcircuit

Data_in <= Data_bus; -- reading data from the input FIFO

Design Entity

Example: NAND Gate

 

a	b	z
0	0	1
0	1	1
1	0	1
1	1	0

Example VHDL Code

- 3 sections to a piece of VHDL code
- File extension for a VHDL file is .vhd
- Name of the file is usually the same as the entity name (nand_gate.vhd)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY nand_gate IS  
    PORT (  
        a    : IN STD_LOGIC;  
        b    : IN STD_LOGIC;  
        z    : OUT STD_LOGIC);  
END nand_gate;
```


```
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    z <= a NAND b;  
END model;
```

} LIBRARY DECLARATION

} ENTITY DECLARATION

} ARCHITECTURE BODY

Design Entity

 


Design Entity - most basic building block of a design.


One *entity* can have many different *architectures*.

Entity Declaration

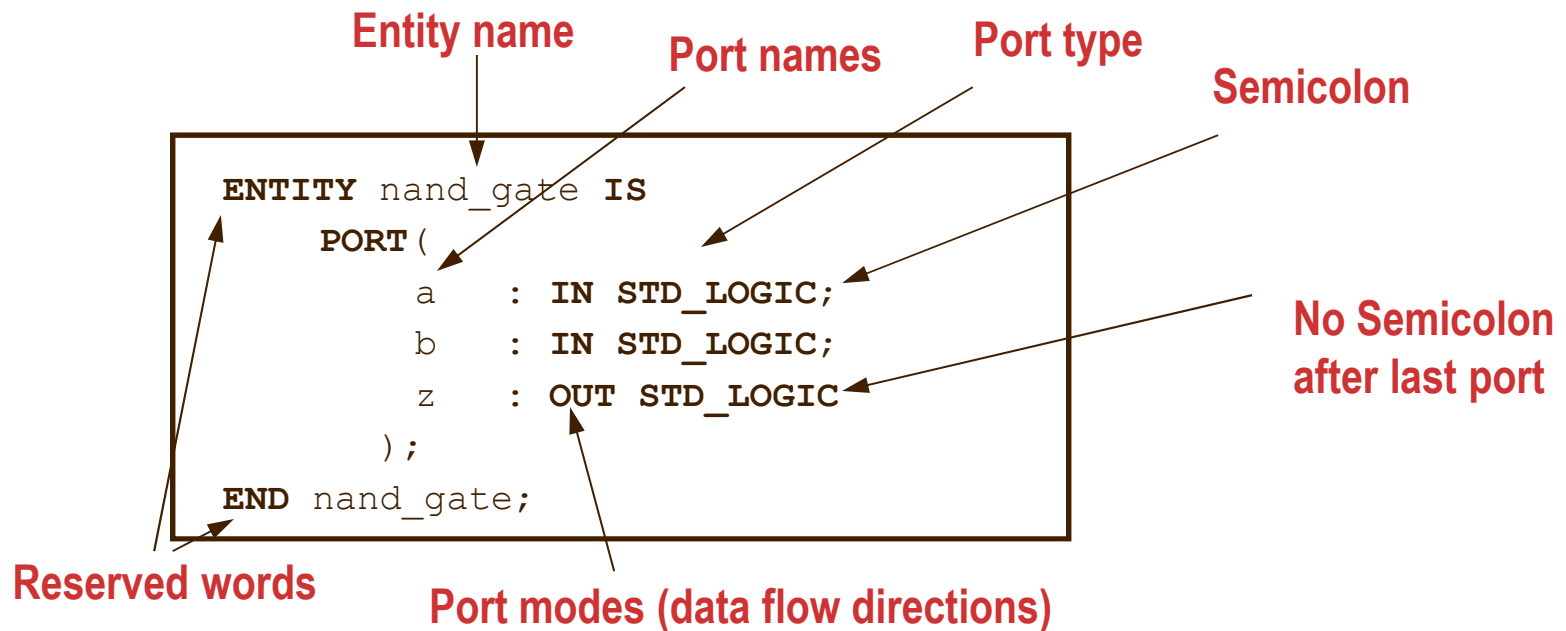
- Entity Declaration describes the interface of the component, i.e. input and output ports.



Port Mode IN

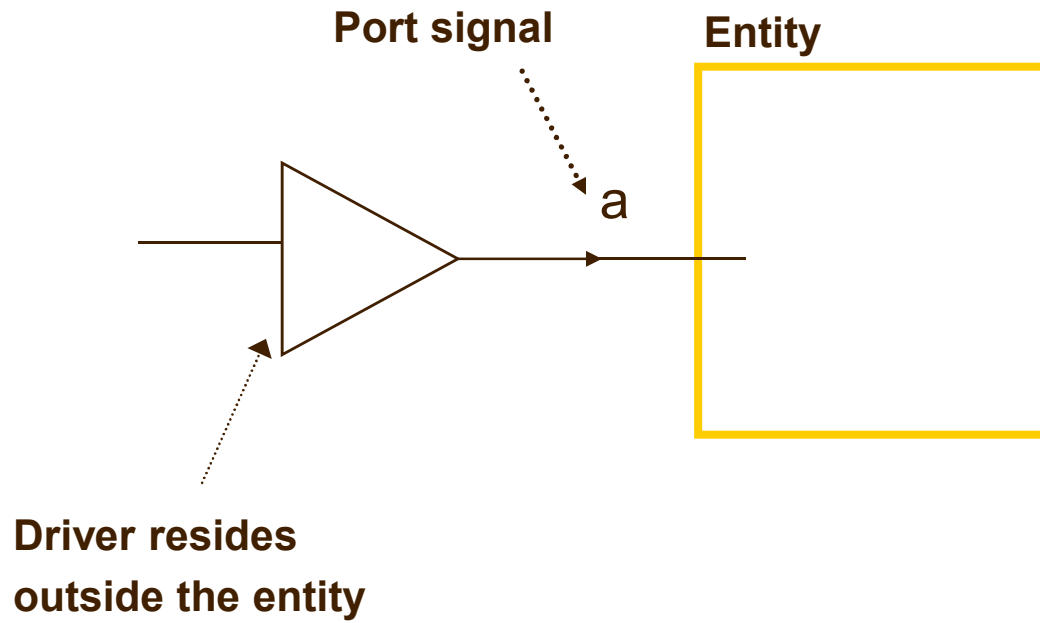

Port Mode OUT

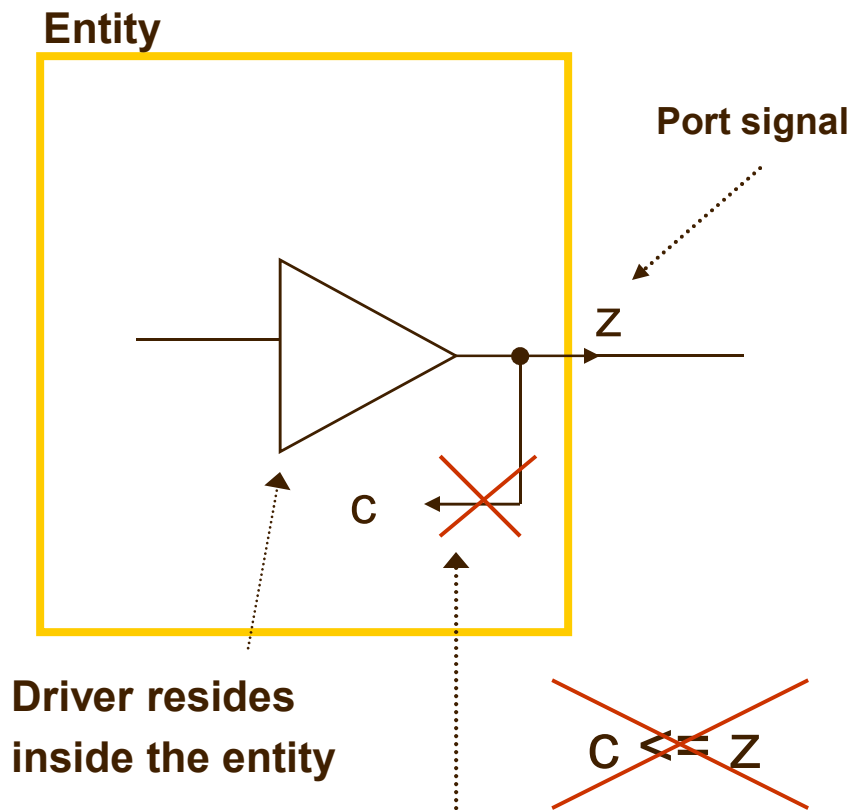

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY nand_gate IS PORT(
    a,b : IN STD_LOGIC;
    c,d : OUT STD_LOGIC);
END nand_gate;


ARCHITECTURE model OF nand_gate IS

BEGIN
    c <= a AND b;
    d <= c and b;
END model;
```

Output cannot be read within the entity

Port Mode OUT (with extra signal)

Entity

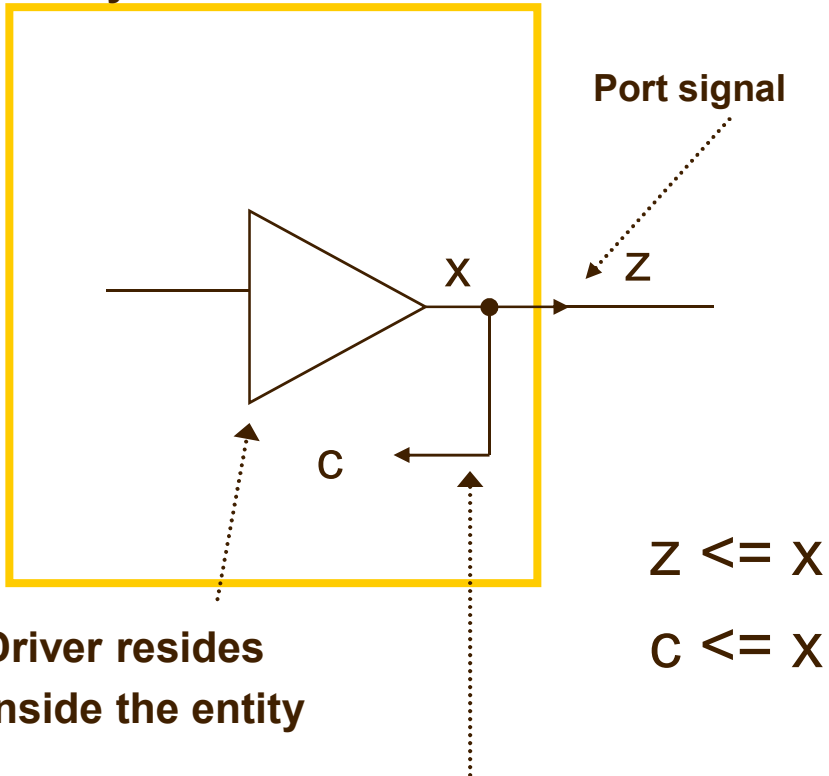

Driver resides
inside the entity


Signal x can be
read inside the entity

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY nand_gate IS PORT(
    a,b : IN STD_LOGIC;
    c,d : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
    signal e: STD_LOGic;

BEGIN
    e <= a AND b;
    c <= e;
    d <= e and b;
END model;
```

Port Mode INOUT

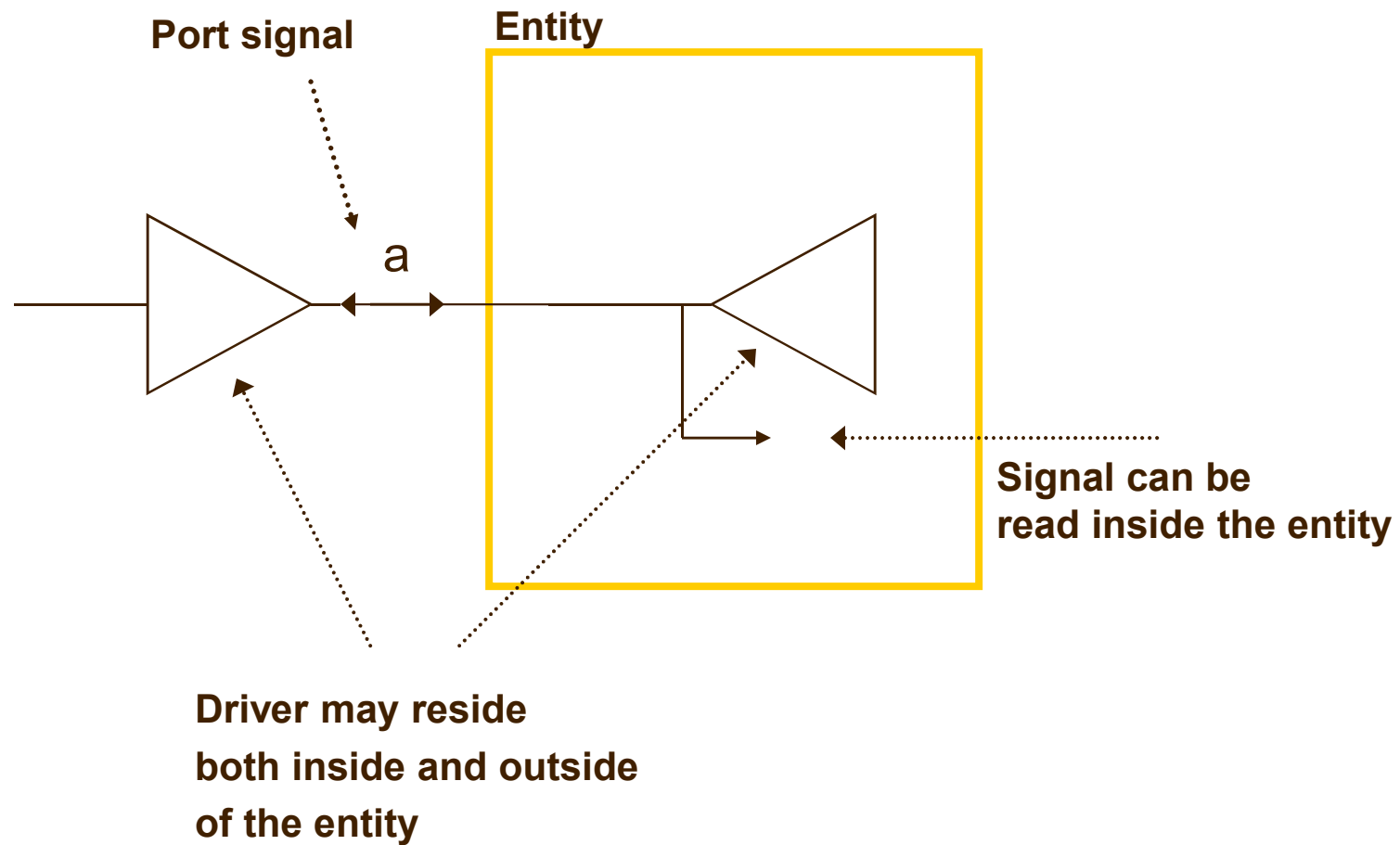

Architecture (*Architecture body*)

- Describes an implementation of a design entity

```
ARCHITECTURE architecture_name OF entity_name IS
  [ declarations ]
BEGIN
  code
END architecture_name;
```

- Architecture example:

```
ARCHITECTURE model OF nand_gate IS
BEGIN
  z <= a NAND b;
END model;
```

Entity Declaration & Architecture

nand_gate.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        a    : IN STD_LOGIC;
        b    : IN STD_LOGIC;
        z    : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE dataflow OF nand_gate IS
BEGIN
    z <= a NAND b;
END dataflow;
```

Library declarations


```
LIBRARY library_name;  
USE library_name.package_name.package_parts;
```

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY nand_gate IS  
    PORT (  
        a    : IN STD_LOGIC;  
        b    : IN STD_LOGIC;  
        z    : OUT STD_LOGIC);  
END nand_gate;  
  
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    z <= a NAND b;  
END model;
```

Library declaration

Use all definitions from the package
std_logic_1164

Parts of a library

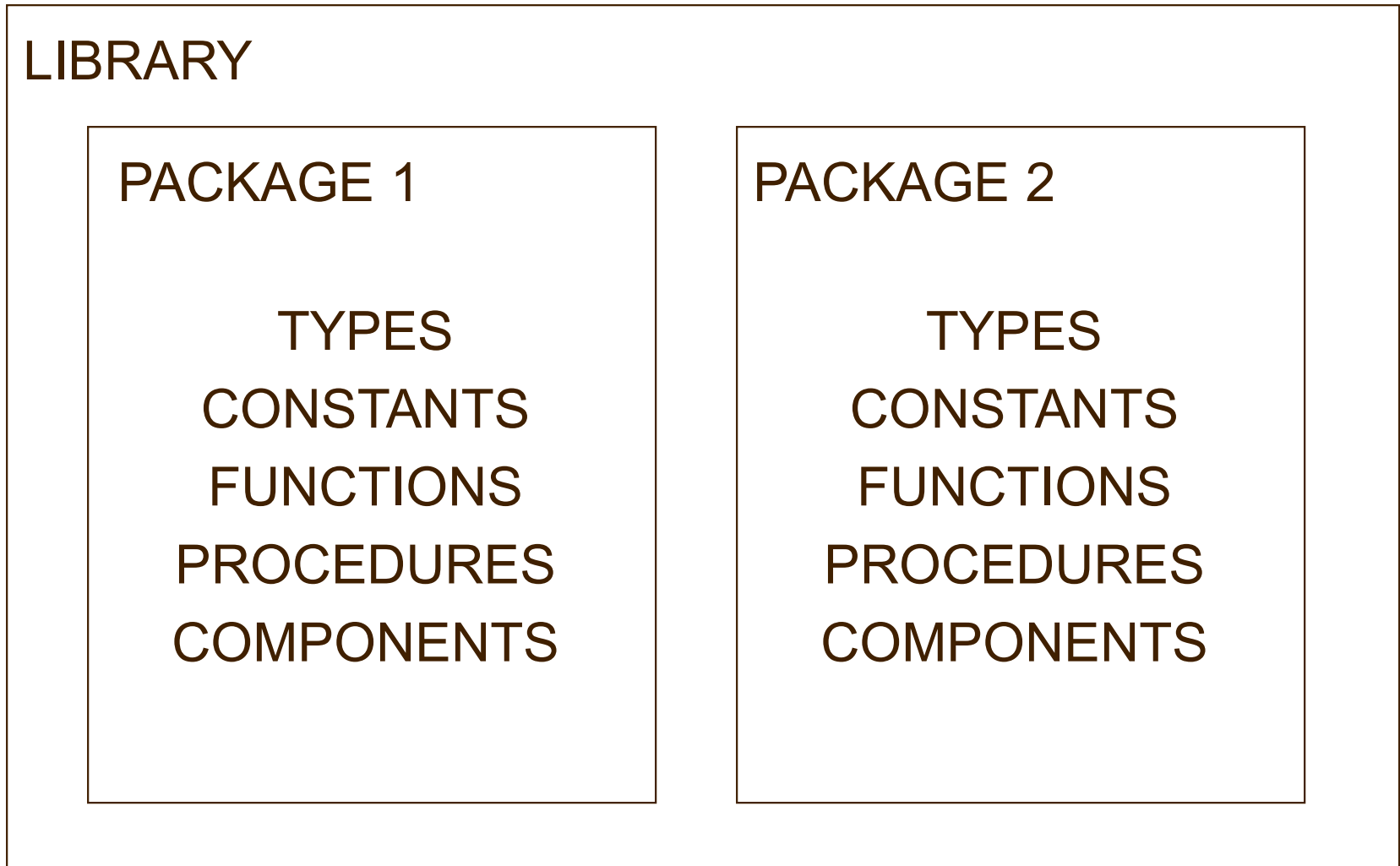

Libraries

- **ieee**

Specifies multi-level logic system, including STD_LOGIC, and STD_LOGIC_VECTOR data types

Need to be explicitly declared

- **std**

Specifies pre-defined data types (BIT, BOOLEAN, INTEGER, REAL, SIGNED, UNSIGNED, etc.), arithmetic operations, basic type conversion functions, basic text i/o functions, etc.

Visible by default

- **work**

Holds current designs after compilation

Bit vs STD_LOGIC

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY nand_gate IS
    PORT (
        a    : IN bit;
        b    : IN bit;
        z    : OUT bit);
END nand_gate;

ARCHITECTURE dataflow OF nand_gate IS
BEGIN
    z <= a NAND b;
END dataflow;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        a    : IN STD_LOGIC;
        b    : IN STD_LOGIC;
        z    : OUT STD_LOGIC);
END nand_gate;

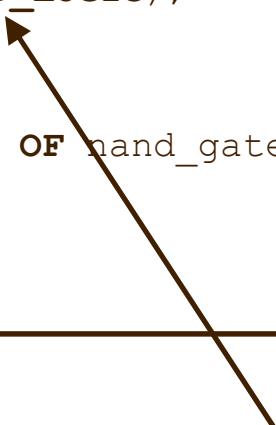ARCHITECTURE dataflow OF nand_gate IS
BEGIN
    z <= a NAND b;
END dataflow;
```




What is **STD_LOGIC**?

BIT versus STD_LOGIC


- BIT type can have a value of '0' or '1'
- STD_LOGIC can have eight values
 - '0', '1', 'X', 'Z', 'W', 'L', 'H', '-'
 - Useful mainly for simulation
 - '0', '1', and 'Z' are synthesizable
 - What is 'X', 'Z';

STD_LOGIC: 'X' vs 'Z'

X

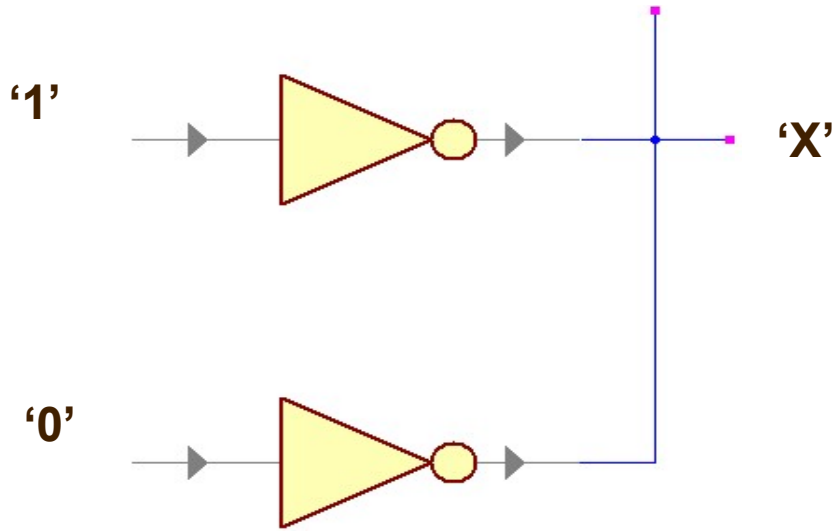


Contention on the bus

 


Signals

SIGNAL a : STD_LOGIC;

 

SIGNAL b : STD_LOGIC_VECTOR(7 DOWNTO 0);

 


Standard Logic Vector examples

```
SIGNAL a: STD_LOGIC;  
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL c: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL d: STD_LOGIC_VECTOR(15 DOWNTO 0);  
SIGNAL e: STD_LOGIC_VECTOR(8 DOWNTO 0);  
  
.....  
  
a <= '1';  
b <= "0000";      -- Binary base assumed by default  
c <= B"0000";    -- Binary base explicitly specified  
d <= X"AF67";    -- Hexadecimal base  
e <= O"723";     -- Octal base
```

Vectors and Concatenation


```
SIGNAL a: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL b: STD_LOGIC_VECTOR(3 DOWNTO 0);  
SIGNAL c, d, e: STD_LOGIC_VECTOR(7 DOWNTO 0);  
  
a <= "0000";  
b <= "1111";  
c <= a & b;           -- c = "00001111"  
  
d <= '0' & "0001111"; -- d <= "00001111"  
  
e <= '0' & '0' & '0' & '0' & '1' & '1' &  
    '1' & '1';  
                                -- e <= "00001111"
```

VHDL Design Styles

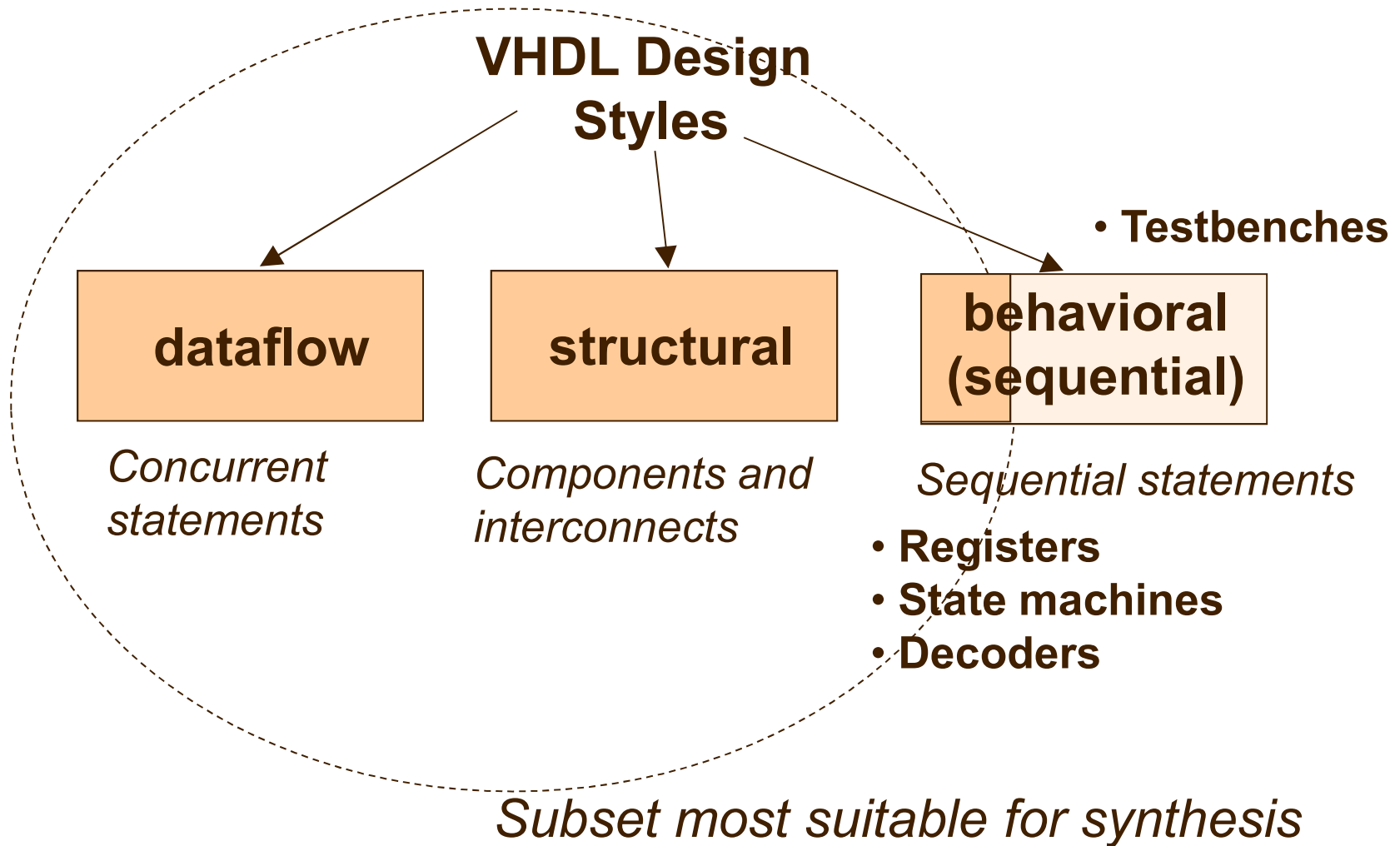

xor3 Example
 
```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
ENTITY xor3_gate IS PORT (  
    A : IN STD_LOGIC;  
    B : IN STD_LOGIC;  
    C : IN STD_LOGIC;  
    Result : OUT STD_LOGIC);  
end xor3_gate;  
ARCHITECTURE df OF xor3_gate IS  
    SIGNAL U1_OUT: STD_LOGIC;  
BEGIN  
    U1_OUT <= A XOR B;  
    Result <= U1_OUT XOR C;  
END dataflow;
```



Dataflow Description

- Describes how data moves through the system and the various processing steps.
 - Dataflow uses series of concurrent statements to realize logic.
 - Dataflow is most useful style when series of Boolean equations can represent a logic → used to implement simple combinational logic
 - Dataflow code also called “concurrent” code
- **Concurrent statements are evaluated at the same time; thus, the order of these statements doesn't matter**

This ...

```
U1_out <= A XOR B;  
Result <= U1_out XOR C;
```

Is the same as this ...

```
Result <= U1_out XOR C;  
U1_out <= A XOR B;
```

Structural architecture - xor2

xor2.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY xor2 IS
    PORT (
        I1    : IN STD_LOGIC;
        I2    : IN STD_LOGIC;
        Y     : OUT STD_LOGIC);
END xor2;

ARCHITECTURE dataflow OF xor2 IS
BEGIN
    Y <= I1 xor I2;
END dataflow;
```

Structural Architecture in VHDL 87

```
ARCHITECTURE structural OF xor3_gate IS
```

```
SIGNAL U1_OUT: STD_LOGIC;
```

```
COMPONENT xor2
```

```
  PORT (
```

```
    I1 : IN STD_LOGIC;
```

```
    I2 : IN STD_LOGIC;
```

```
    Y  : OUT STD_LOGIC
```

```
  );
```



```
END COMPONENT;
```

```
BEGIN
```

```
  U1: xor2 PORT MAP (I1 => A,  
                    I2 => B,  
                    Y  => U1_OUT);
```

```
  U2: xor2 PORT MAP (I1 => U1_OUT,  
                    I2 => C,  
                    Y  => Result);
```

```
END structural;
```

  

PORT NAME

LOCAL WIRE NAME

Structural Description

- Structural design is the simplest to understand. This style is the closest to schematic capture and utilizes simple building blocks to compose logic functions.
- Components are interconnected in a hierarchical manner.
- Structural descriptions may connect simple gates or complex, abstract components.
- Structural style is useful when expressing a design that is naturally composed of sub-blocks.

Behavioral Architecture (xor3 gate)

```
ARCHITECTURE behavioral OF xor3 IS  
BEGIN  
xor3_behave: PROCESS (A, B, C)  
BEGIN  
    IF ((A XOR B XOR C) = '1') THEN  
        Result <= '1';  
    ELSE  
        Result <= '0';  
    END IF;  
END PROCESS xor3_behave;  
END behavioral;
```

Behavioral Description

- It accurately models what happens on the inputs and outputs of the black box (no matter what is inside and how it works).
- This style uses `PROCESS` statements in *VHDL*.