



ΠΑΝΕΠΙΣΤΗΜΙΟ ΔΥΤΙΚΗΣ ΑΤΤΙΚΗΣ

ΣΧΟΛΗ ΜΗΧΑΝΙΚΩΝ

ΤΜΗΜΑ ΜΗΧΑΝΙΚΩΝ ΠΛΗΡΟΦΟΡΙΚΗΣ ΚΑΙ ΥΠΟΛΟΓΙΣΤΩΝ

# Πρόγραμμα Μεταπτυχιακών Σπουδών «Πληροφορική και Εφαρμογές»



**Αρχές Ψηφιακής Τεχνολογίας**  
Εισαγωγή στη VHDL  
Γιάννης Βογιατζής  
2018-2019

# VHDL

---

- VHDL: γλώσσα περιγραφής υλικού
  - **VHDL** : **V**HSIC (**V**ery **H**igh **S**peed **I**ntegrated **C**ircuit) **H**ardware **D**escription **L**anguage

# Naming and Labeling (1)

---

- VHDL is case insensitive

Example:

Names or labels

**databus**

**Databus**

**DataBus**

**DATABUS**

are all equivalent

# Naming and Labeling (2)

---

1. Τα ονόματα αρχίζουν από (a-z or A-Z)
2. Χρησιμοποιούνται χαρακτήρες (a-z or A-Z) ψηφία (0-9) και underscore (\_)
3. Δε χρησιμοποιούνται punctuation ή reserved characters (!, ?, ., &, +, -, etc.)
4. Δε χρησιμοποιούνται δύο ή περισσότερα underscore characters (\_\_)
5. Όλα τα ονόματα σε ένα entity πρέπει να είναι μοναδικά

# Free Format

---

- Η Vhdl είναι “free format” γλώσσα

Example:

```
if (a=b) then
```

*or*

```
if (a=b)           then
```

*or*

```
if (a =  
b) then
```

are all equivalent

# Σχόλια

---

- Με “double dash”, i.e., “--”
  - Μπορούν να μπουν οπουδήποτε στη γραμμή
  - Ότι είναι στην ίδια γραμμή είναι σχόλιο

Examples:

-- main subcircuit

Data\_in <= Data\_bus;    -- reading data from the input FIFO

# Example VHDL Code

---

- 3 sections to a piece of VHDL code
- File extension for a VHDL file is .vhd
- Name of the file **should be** the same as the entity name (nand\_gate.vhd)

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY nand_gate IS  
    PORT (  
        a    : IN BIT;  
        b    : IN BIT;  
        z    : OUT BIT);
```

```
END nand_gate;
```

```
ARCHITECTURE model OF nand_gate IS  
BEGIN  
    z <= a NAND b;  
END model;
```

} LIBRARY DECLARATION


} ENTITY DECLARATION

} ARCHITECTURE BODY
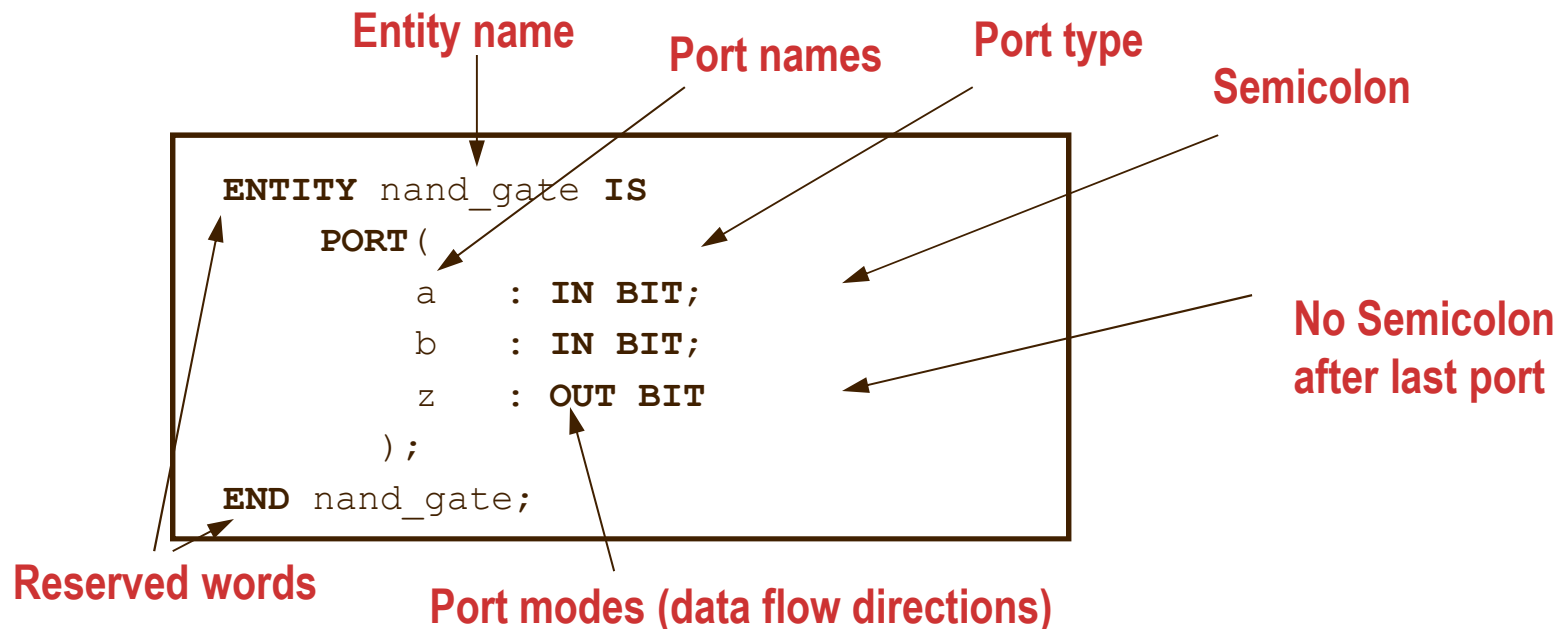
# Entity Declaration


---

- Entity Declaration describes the interface of the component, i.e. input and output ports.




# Port Mode IN

---

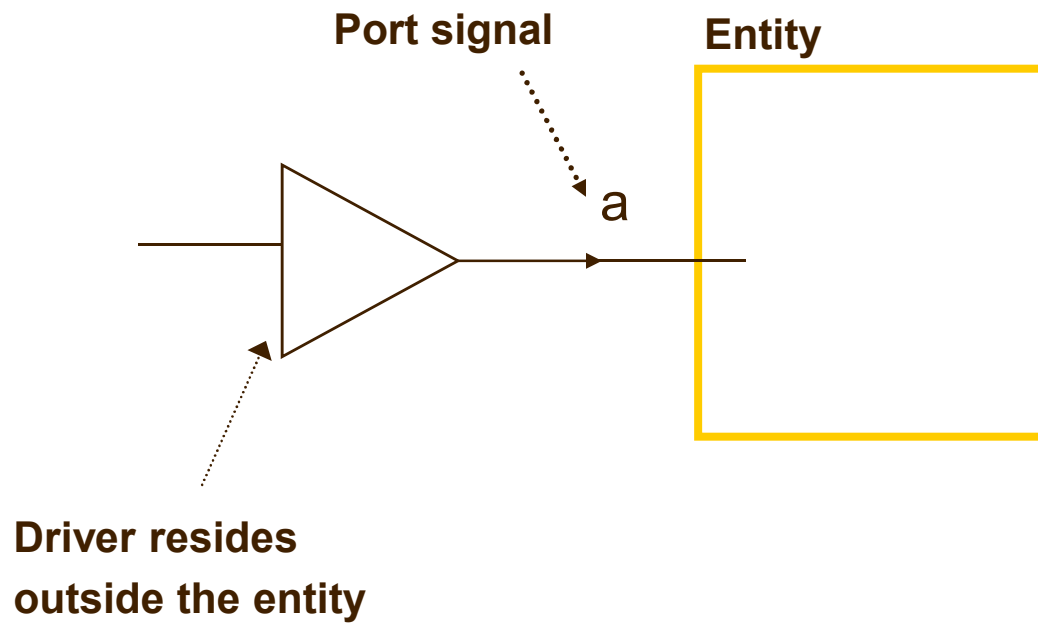


# Port Mode OUT

---

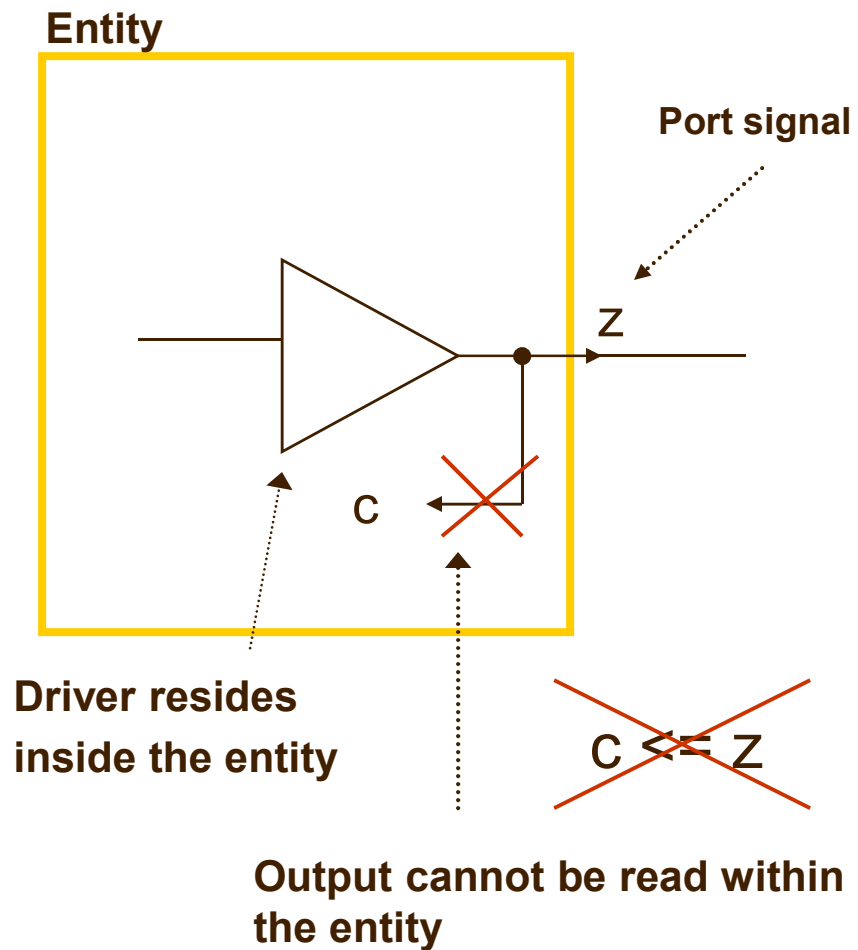

# Port Mode OUT

---

 


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY nand_gate IS PORT(
    a,b : IN BIT;
    c,d : OUT BIT);
END nand_gate;
```

```
ARCHITECTURE model OF nand_gate IS
```

```
BEGIN
    c <= a AND b;
    d <= c and b;
END model;
```

# Port Mode OUT (with extra signal)

---

 

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
ENTITY nand_gate IS PORT(  
    a,b : IN BIT;  
    c,d : OUT BIT);  
END nand_gate;
```

```
ARCHITECTURE model OF nand_gate IS  
    signal e: BIT;
```

```
BEGIN  
    e <= a AND b;  
    c <= e;  
    d <= e and b;  
END model;
```

# *Architecture (Architecture body)*

---

- Describes an implementation of a design entity
- Architecture example:

```
ARCHITECTURE model OF nand_gate IS
BEGIN
    z <= a NAND b;
END model;
```

# Library Declarations

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        a    : IN BIT;
        b    : IN BIT;
        z    : OUT BIT);
END nand_gate;

ARCHITECTURE model OF nand_gate IS
BEGIN
    z <= a NAND b;
END model;
```


Library declaration

Use all definitions from the package  
std\_logic\_1164


# Signals

---

SIGNAL a : BIT;

 

SIGNAL b : BIT\_VECTOR(7 DOWNTO 0);

 

# Standard Logic Vector examples

---

```
SIGNAL a: BIT;
SIGNAL b: BIT_VECTOR(3 DOWNT0 0);
SIGNAL c: BIT_VECTOR(3 DOWNT0 0);
SIGNAL d: BIT_VECTOR(15 DOWNT0 0);
SIGNAL e: BIT_VECTOR(8 DOWNT0 0);

.....

a <= '1';
b <= "0000";      -- Binary base assumed by default
c <= B"0000";    -- Binary base explicitly specified
d <= X"AF67";    -- Hexadecimal base
e <= O"723";     -- Octal base
```

# Vectors and Concatenation

---

```
SIGNAL a: BIT_VECTOR(3 DOWNTO 0);
SIGNAL b: BIT_VECTOR(3 DOWNTO 0);
SIGNAL c, d, e: BIT_VECTOR(7 DOWNTO 0);


a <= "0000";
b <= "1111";
c <= a & b;
-- c = "00001111"

d <= '0' & "0001111";
-- d <= "00001111"

e <= '0' & '0' & '0' & '0' & '1' & '1' & '1' & '1';
-- e <= "00001111"
```


# VHDL Design Styles

---

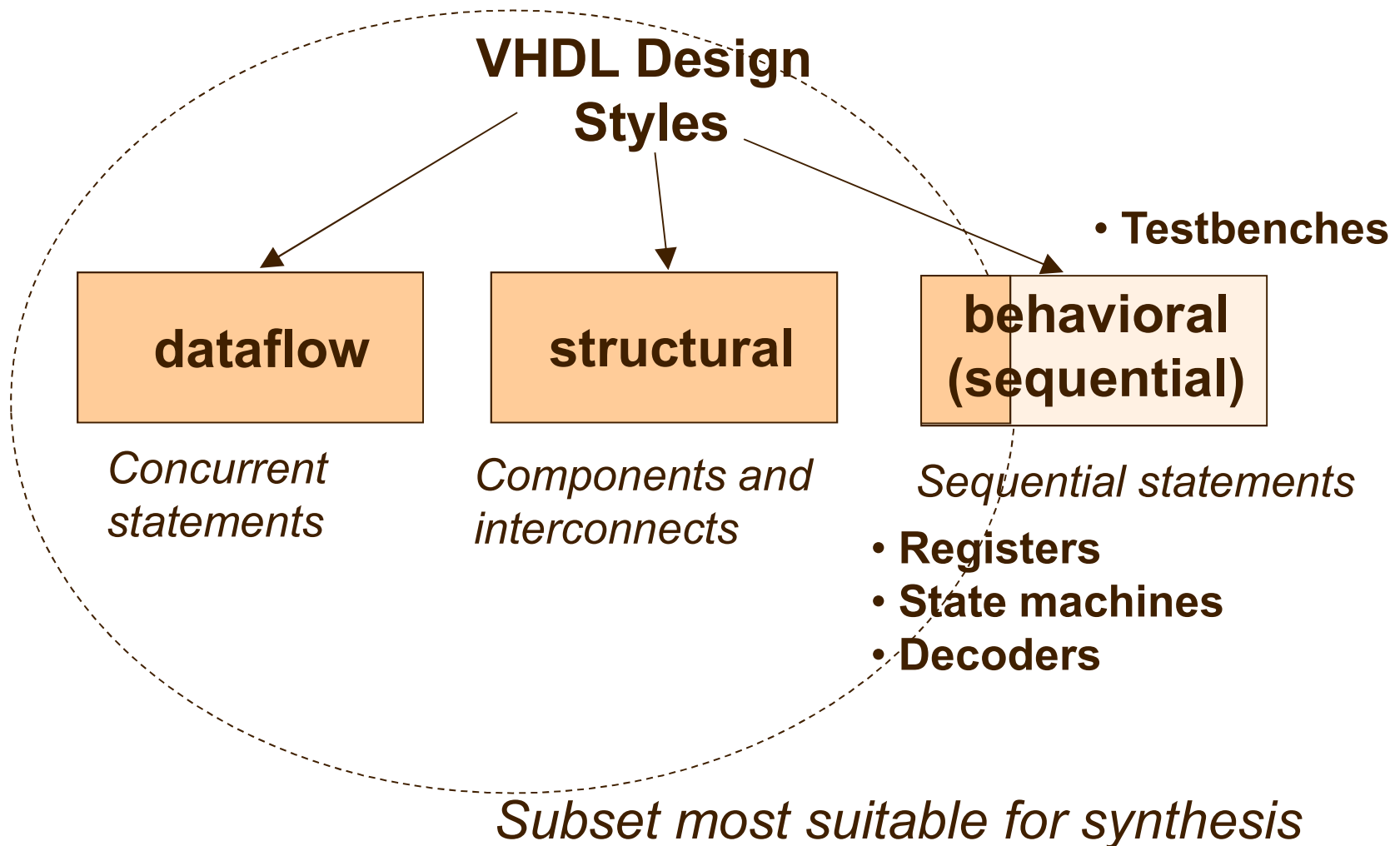

# xor3 Example

---

 

# Entity xor3\_gate

---

```
LIBRARY ieee;
```

```
USE ieee.std_logic_1164.all;
```

```
ENTITY xor3_gate IS PORT (
```

```
    A : IN BIT;
```

```
    B : IN BIT;
```

```
    C : IN BIT;
```


```
    Result : OUT BIT);
```

```
end xor3_gate;
```
 
# Dataflow Architecture (xor3\_gate)

---

```
ARCHITECTURE dataflow OF xor3_gate IS  
SIGNAL U1_OUT: BIT;  
BEGIN  
    U1_OUT <= A XOR B;  
    Result <= U1_OUT XOR C;  
END dataflow;
```



# Dataflow Description

---

- Περιγράφει πώς μετακινούνται τα data στο σύστημα.
  - Σειρά από concurrent statements
  - Χρήσιμο όταν μια σειρά από Boolean συναρτήσεις αναπαριστούν τη λογική →
    - χρησιμοποιείται για απλή συνδυαστική λογική
  - Ο Dataflow κώδικας ονομάζεται και “concurrent” κώδικας
- **Concurrent statements: αξιολογούνται ταυτόχρονα**
- **Έτσι, η σειρά δεν παίζει ρόλο**

This ...

```
U1_out <= A XOR B;  
Result <= U1_out XOR C;
```

Is the same as this ...

```
Result <= U1_out XOR C;  
U1_out <= A XOR B;
```

# Structural Description

---

- Structural design είναι η πιο κοντινή περιγραφή στο schematic capture.
- Τα Components διασυνδέονται με ιεραρχικό τρόπο.
- Μπορεί να διασυνδέει απλές πύλες ή πολύπλοκες μονάδες.
- Χρήσιμο όταν περιγράφουμε μονάδες που αποτελούνται από υπομονάδες.

# Structural architecture - xor2

---

xor2.vhd

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY xor2 IS
    PORT (
        I1    : IN BIT;
        I2    : IN BIT;
        Y     : OUT BIT);
END xor2;

ARCHITECTURE dataflow OF xor2 IS
BEGIN
    Y <= I1 xor I2;
END dataflow;
```

# Structural Architecture

```
ARCHITECTURE structural OF xor3_gate IS
```

```
SIGNAL U1_OUT: BIT;
```

```
COMPONENT xor2
```

```
  PORT (
```

```
    I1 : IN BIT;
```

```
    I2 : IN BIT;
```

```
    Y  : OUT BIT
```

```
  );
```

```
END COMPONENT;
```


```
BEGIN
```

```
  U1: xor2 PORT MAP (I1 => A,  
                    I2 => B,  
                    Y  => U1_OUT);
```

```
  U2: xor2 PORT MAP (I1 => U1_OUT,  
                    I2 => C,  
                    Y  => Result);
```

```
END structural;
```
 
```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
ENTITY xor2 IS PORT(  
    I1    : IN BIT;  
    I2    : IN BIT;  
    Y     : OUT BIT);  
END xor2;  
ARCHITECTURE dataflow OF xor2 IS  
BEGIN  
    Y <= I1 xor I2;  
END dataflow;
```



PORT NAME

LOCAL WIRE NAME

# Behavioral Architecture (xor3 gate)

---

```
ARCHITECTURE behavioral OF xor3 IS  
BEGIN  
xor3_behave: PROCESS (A, B, C)  
BEGIN  
    IF ((A XOR B XOR C) = '1') THEN  
        Result <= '1';  
    ELSE  
        Result <= '0';  
    END IF;  
END PROCESS xor3_behave;  
END behavioral;
```

# Behavioral Description

---

- Περιγράφει τι συμβαίνει μεταξύ των εισόδων και εξόδων σα να είναι μαύρο κουτί
- Χρησιμοποιεί PROCESS statements.

# STD\_LOGIC

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY nand_gate IS
    PORT (
        a    : IN STD_LOGIC;
        b    : IN STD_LOGIC;
        z    : OUT STD_LOGIC);
END nand_gate;

ARCHITECTURE dataflow OF nand_gate IS
BEGIN
    z <= a NAND b;
END dataflow;
```

What is **STD\_LOGIC**?


# BIT versus STD\_LOGIC

---

- BIT type can only have a value of '0' or '1'
- STD\_LOGIC can have eight values
  - '0', '1', 'X', 'Z', 'W', 'L', 'H', '-'
  - Useful mainly for simulation
  - '0', '1', and 'Z' are synthesizable
- What is 'X', 'Z';


# STD\_LOGIC: 'X'

---

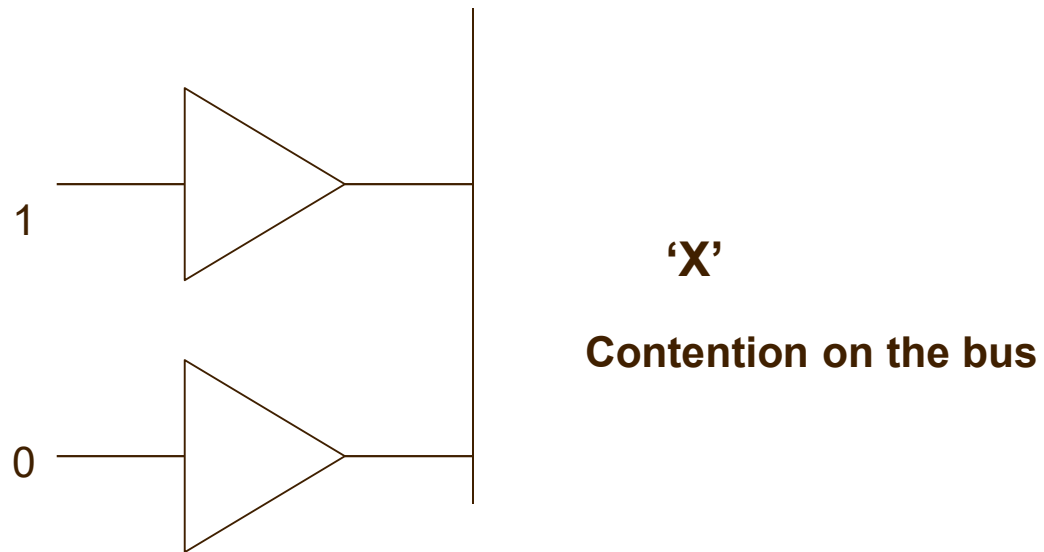

# STD\_LOGIC: 'Z'


---

 



Tristate buffer

Πώς φτιάχνω ένα Tristate buffer??

# Tri-state Buffer

 

(a) A tri-state buffer

  


(b) Equivalent circuit

$e$	$x$	$f$
0	0	Z
0	1	Z
1	0	0
1	1	1


(c) Truth table

# Four types of Tri-state Buffers


---

 


(a)

 

(b)

 


(c)

 


(d)


# Four types of Tri-state Buffers

 
 
```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```


 
```
ENTITY tri_state IS PORT (
    e: IN STD_LOGIC;
    input: IN STD_LOGIC;
    output: OUT STD_LOGIC);
END tri_state;
```



```
ARCHITECTURE dataflow OF tri_state IS
BEGIN
    output <= input WHEN (e = '1')
        ELSE 'Z';
END dataflow;
```

