



ΠΑΝΕΠΙΣΤΗΜΙΟ ΔΥΤΙΚΗΣ ΑΤΤΙΚΗΣ

ΣΧΟΛΗ ΜΗΧΑΝΙΚΩΝ

ΤΜΗΜΑ ΜΗΧΑΝΙΚΩΝ ΠΛΗΡΟΦΟΡΙΚΗΣ ΚΑΙ ΥΠΟΛΟΓΙΣΤΩΝ

Πρόγραμμα Μεταπτυχιακών Σπουδών «Πληροφορική και Εφαρμογές»

Αρχές Ψηφιακής Τεχνολογίας

Γιάννης Βογιατζής
2018-2019




Προσομοίωση λειτουργίας

```
library IEEE;  
use ieee.std_logic_1164.all;  
use ieee.std_logic_unsigned.all;  
  
entity mux21 is port  
  (a, b, s: in bit;  
    c: out bit);  
end mux21;  
  
architecture struct1 of mux21 is  
  begin  
    c <= (a and s) or (b and not s);  
end struct1;
```

Προσομοίωση λειτουργίας


```
entity test_mux is  
end test_mux;  
  
architecture test_b of test_mux is  
signal A1, B1, S1, C1: bit;  
component mux21 port (a, b, s: in bit; c: out bit);  
end component;  
  
begin  
M1: mux21 PORT MAP (a=>A1, b=>B1, s=>s1, c=>c1);  
process  
  begin  
    A1 <= '1'; B1 <= '0'; S1 <= '1'; wait for 20 ns;  
    A1 <= '1'; B1 <= '0'; S1 <= '0'; wait for 20 ns;  
  end process;  
end test_b;
```

Merging wires and buses

 

```
SIGNAL a: BIT_VECTOR(3 DOWNT0 0);  
SIGNAL b: BIT_VECTOR(4 DOWNT0 0);  
SIGNAL c: BIT;  
SIGNAL d: BIT_VECTOR(9 DOWNT0 0);  
  
d <= a & b & c;
```

Splitting buses

 

```
SIGNAL a: BIT_VECTOR(3 DOWNTO 0);  
SIGNAL b: BIT_VECTOR(4 DOWNTO 0);  
SIGNAL c: BIT;  
SIGNAL d: BIT_VECTOR(9 DOWNTO 0);  
  
a <= d(9 downto 6);  
b <= d(5 downto 1);  
c <= d(0);
```

Operators

- Relational operators


=	/=	<	<=	>	>=
---	----	---	----	---	----

- Logic and relational operators precedence

Highest
↓
Lowest

=	/=	<	<=	>	>=
and	or	nand	nor	xor	xnor


Data-flow VHDL Example 1: Full adder

 

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
ENTITY fulladd IS PORT (  
    x      : IN BIT;  
    y      : IN BIT;  
    cin    : IN BIT;  
    s      : OUT BIT;  
    cout   : OUT BIT);  
END fulladd ;
```

```
ARCHITECTURE dataflow OF fulladd IS  
BEGIN  
    s      <= x XOR y XOR cin;  
    cout   <= (x AND y) OR (cin AND x) OR (cin AND y);  
END dataflow ;
```

Χρήση της δομής when: 2-to-1 Multiplexer

 

Graphical symbol

<i>s</i>	<i>f</i>
0	<i>w</i> ₀
1	<i>w</i> ₁


Truth table

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;
```

```
ENTITY mux2to1 IS PORT (  
    w0, w1, s: IN STD_LOGIC;  
    f: OUT STD_LOGIC);  
END mux2to1 ;
```

```
ARCHITECTURE dataflow OF mux2to1 IS  
BEGIN  
    f <= w0 WHEN s = '0' ELSE w1;  
END dataflow;
```

 Χρήση της δομής with select: 4-to-1 Multiplexer



Graphic symbol

operation table

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY mux4to1 IS PORT (
  w0, w1, w2, w3: IN BIT;
  s: IN BIT_VECTOR(1 DOWNTO 0);
  f: OUT BIT);
END mux4to1 ;
```


```
ARCHITECTURE dataflow OF mux4to1 IS
BEGIN
  WITH s SELECT
    f <= w0 WHEN "00",
        w1 WHEN "01",
        w2 WHEN "10",
        w3 WHEN OTHERS;
END dataflow ;
```

Ποια είναι τα others?

2-to-4 Decoder with enable

En	w_1	w_0	y_3	y_2	y_1	y_0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0
0	x	x	0	0	0	0

(a) Truth table

 

(b) Graphical symbol

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY dec2to4 IS PORT (
    w : IN BIT_VECTOR(1 DOWNTO 0);
    En: IN BIT;
    y : OUT BIT_VECTOR(3 DOWNTO 0));
END dec2to4;

ARCHITECTURE dataflow OF dec2to4 IS
    SIGNAL Enw: BIT_VECTOR(2 DOWNTO 0);
BEGIN
    Enw <= En & w ;
    WITH Enw SELECT
        y <= "0001" WHEN "100",
            "0010" WHEN "101",
            "0100" WHEN "110",
            "1000" WHEN "111",
            "0000" WHEN OTHERS ;
END dataflow ;
    
```

Arithmetic Operators in VHDL


To use basic arithmetic operations involving `std_logic_vectors` you need to include the following library packages:

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_unsigned.all;  
or  
USE ieee.std_logic_signed.all;
```

You can use standard + and - operators to perform addition and subtraction:

```
signal A : BIT_VECTOR(3 downto 0);  
signal B : BIT_VECTOR(3 downto 0);  
signal C : BIT_VECTOR(3 downto 0);  
  
.....  
C <= A + B;
```

VHDL code for a 16-bit Unsigned Adder

 

```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all;  
USE ieee.std_logic_unsigned.all;
```

```
ENTITY adder16 IS PORT (  
  Cin  : IN  STD_LOGIC ;  
  X, Y : IN  STD_LOGIC_VECTOR(15 DOWNTO 0);  
  S    : OUT STD_LOGIC_VECTOR(15 DOWNTO 0);  
  Cout : OUT STD_LOGIC);  
END adder16 ;
```

```
ARCHITECTURE dataflow OF adder16 IS  
  SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNTO 0);  
BEGIN  
  Sum <= ('0' & X) + Y + Cin;  
  S <= Sum(15 DOWNTO 0);  
  Cout <= Sum(16);  
END dataflow;
```

4-bit Unsigned Number Comparator



```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;

ENTITY compare IS PORT (
  A, B : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
  AeqB, AgtB, AltB: OUT STD_LOGIC);
END compare;

ARCHITECTURE dataflow OF compare IS
BEGIN
  AeqB <= '1' WHEN A = B ELSE '0';
  AgtB <= '1' WHEN A > B ELSE '0';
  AltB <= '1' WHEN A < B ELSE '0';
END dataflow;
```

4-bit Signed Number Comparator



```
LIBRARY ieee ;  
USE ieee.std_logic_1164.all ;  
USE ieee.std_logic_signed.all ;
```

```
ENTITY compare IS PORT (  
  A, B: IN STD_LOGIC_VECTOR(3 DOWNT0 0);  
  AeqB, AgtB, AltB: OUT STD_LOGIC);  
END compare;
```

```
ARCHITECTURE dataflow OF compare IS
```

```
BEGIN
```


```
  AeqB <= '1' WHEN  A = B ELSE '0';
```

```
  AgtB <= '1' WHEN  A > B ELSE '0';
```

```
  AltB <= '1' WHEN  A < B ELSE '0';
```

```
END dataflow;
```

Priority Encoder

 

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

```


LIBRARY ieee ;
USE ieee.std_logic_1164.all;

ENTITY priority IS PORT(
    w : IN  STD_LOGIC_VECTOR(3 DOWNTO 0);
    y : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
    z : OUT STD_LOGIC ) ;
END priority;

ARCHITECTURE dataflow OF priority IS
BEGIN
    y <= "11" WHEN w(3) = '1' ELSE
        "10" WHEN w(2) = '1' ELSE
        "01" WHEN w(1) = '1' ELSE
        "00";
    z <= '0' WHEN w = "0000" ELSE '1';
END dataflow;

```

Data-flow VHDL Example 2: MLU module

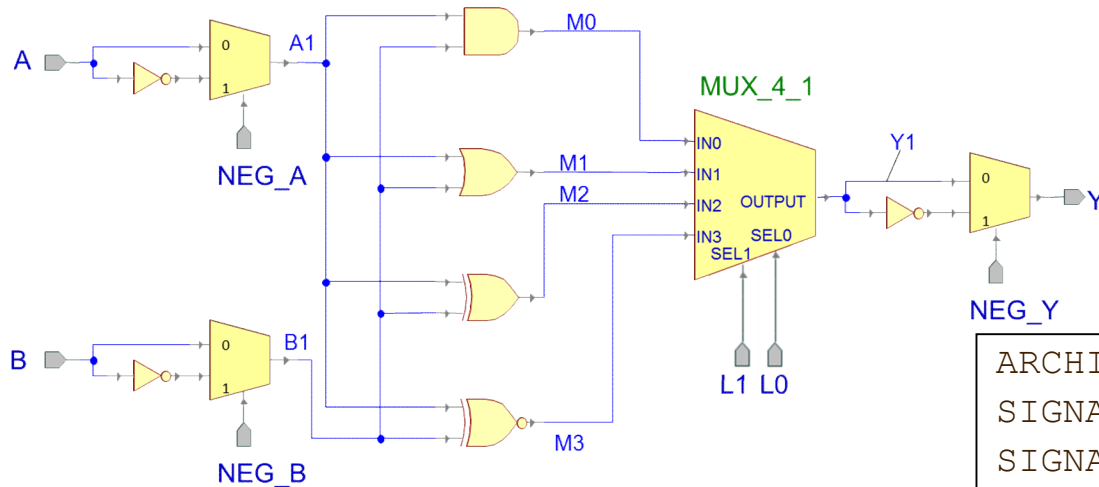

Ποιες εισόδους;
 Ποιες εξόδους;
 Ποια signals;

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mlu IS PORT(
    NEG_A, NEG_B, NEG_Y: IN STD_LOGIC;
    A, B: IN STD_LOGIC;
    L1, L0: IN STD_LOGIC;
    L0: IN STD_LOGIC;
    Y: OUT STD_LOGIC);
END mlu;
    
```


```

ARCHITECTURE mlu_dataflow OF mlu IS
    SIGNAL A1, B1, Y1: STD_LOGIC;
    SIGNAL M0, M1, M2, M3: STD_LOGIC;
    SIGNAL L: STD_LOGIC_VECTOR(1 DOWNTO 0);
BEGIN
    A1<= NOT A  WHEN (NEG_A='1') ELSE A;
    B1<= NOT B  WHEN (NEG_B='1') ELSE B;
    Y <= NOT Y1 WHEN (NEG_Y='1') ELSE Y1;
    M0 <= A1 AND  B1;
    M1 <= A1 OR   B1;
    M2 <= A1 XOR  B1;
    M3 <= A1 XNOR B1;
    L <= L1 & L0;
    with (L) select
    Y1 <=  MUX_0  WHEN "00",
           MUX_1  WHEN "01",
           MUX_2  WHEN "10",
           MUX_3  WHEN OTHERS;
END mlu_dataflow;
    
```

Logic Implied by Conditional and Selected Concurrent Signal Assignments

When - Else

 
```
target_signal <= value1  when condition1 else  
                    value2  when condition2 else  
                    . . .  
                    valueN-1 when conditionN-1 else  
                    valueN;
```



Logic Implied by Conditional and Selected Concurrent Signal Assignments

With –Select-When
 
```
with choice_expression select  
  target_signal <= expression1 when choices_1,  
                    expression2 when choices_2,  
                    . . .  
                    expressionN when choices_N;
```



Allowed formats of *choices_k*

```
WHEN value
```

```
WHEN value_1 | value_2 | ... | value N
```

```
WHEN OTHERS
```

Example

```
WITH sel SELECT  
y <= a WHEN "000",  
    c WHEN "001" | "111",  
    d WHEN OTHERS;
```